

Laborator nr. 3:


Transistorul bipolar:

transistor - permite controlul unui curent folosind un alt curent sau o tensiune


TB, BJT - „Bipolar Junction Transistor”.

BJT - 2 jonctiuni pn sau mp



BJT mpn

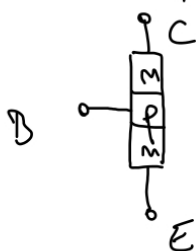


pmn

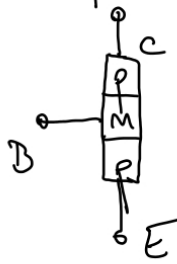

B - baza
C - colector
E - emitor

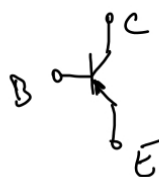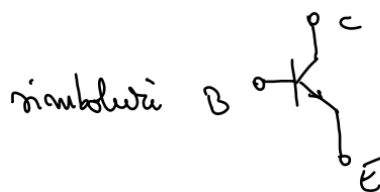

Ex: mpn

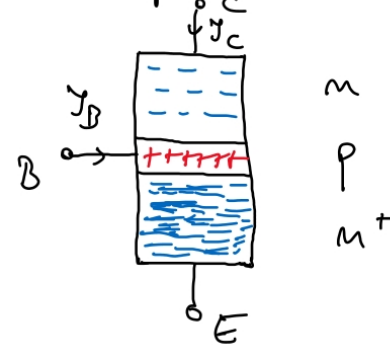


Regimuri de functionare:

- switch electronic (blocat/saturat)
- sursa de curent controlabila (activ)


transistor - cel mai simplu amplificator

scheme echivalente:


blocat

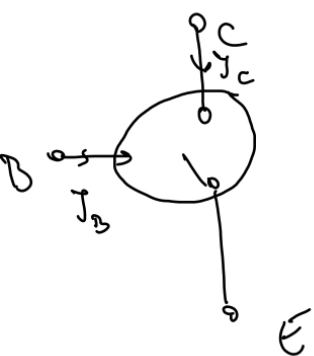

saturat

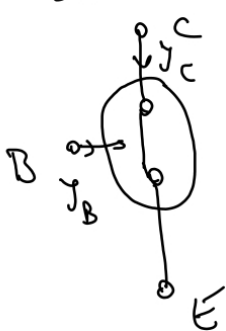

activa


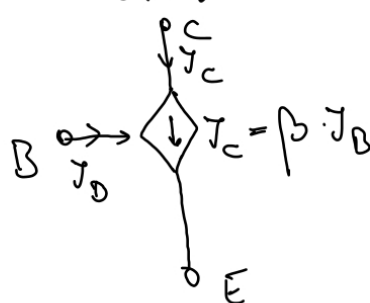


BJT - dispozitiv comandat in curent

$$I_c = \beta \cdot I_b \quad \begin{matrix} I_b \rightarrow \mu A \\ I_c \rightarrow mA \end{matrix}$$

β - factorul de amplificatie

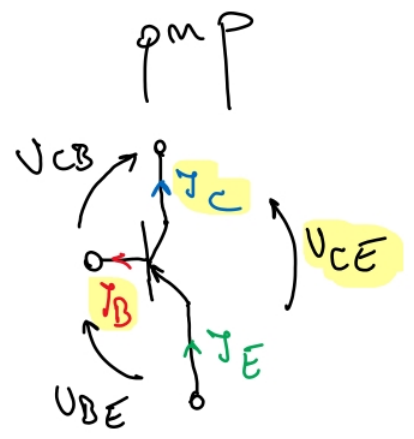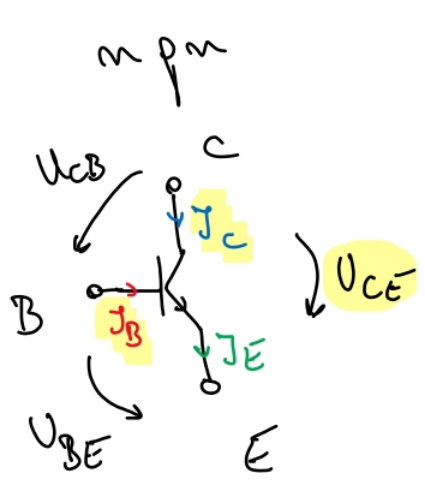
small-signal: $\beta = 100 - 1000$
putere: $\beta = 2 - 10$




Regimuri de funcționare (m p n)

- blocat:
 - $U_{BE} < 0.7V \rightarrow I_B = 0 \rightarrow I_C = 0$
 - $U_{CE} = +E_c$
- activ
 - $U_{BE} \geq 0.7V \rightarrow I_B > 0$
 - $I_C = \beta \cdot I_B$
(liniară)
 - $U_{CE} > 0$
- saturat
 - $U_{BE} \geq 0.7V$
 - $I_B > 0 ; I_C \neq \beta \cdot I_B$
 - $U_{CE} \approx 0 - 0.2V$


Caracteristica joncțiunii BE

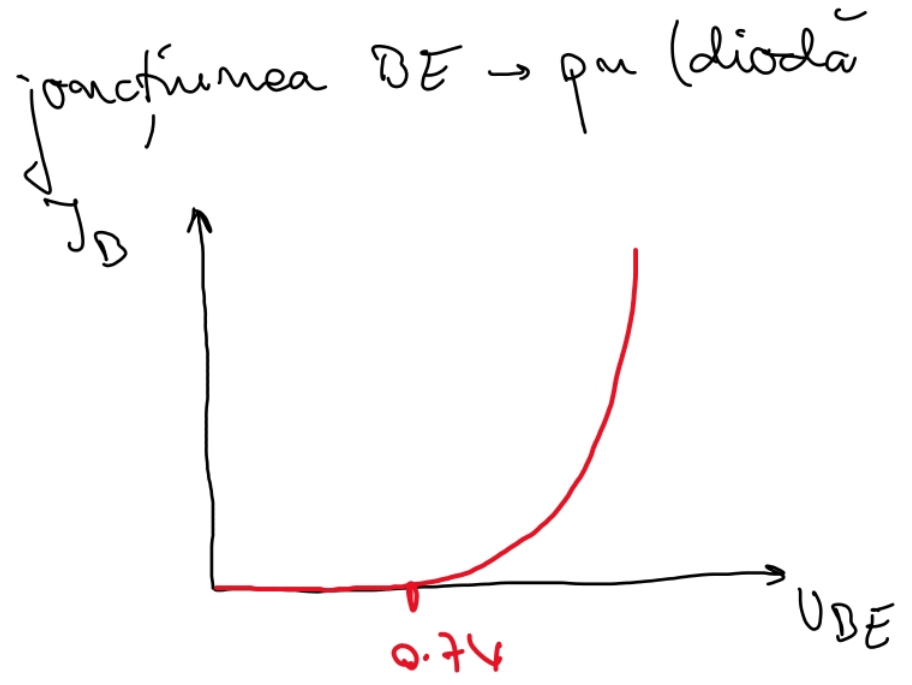


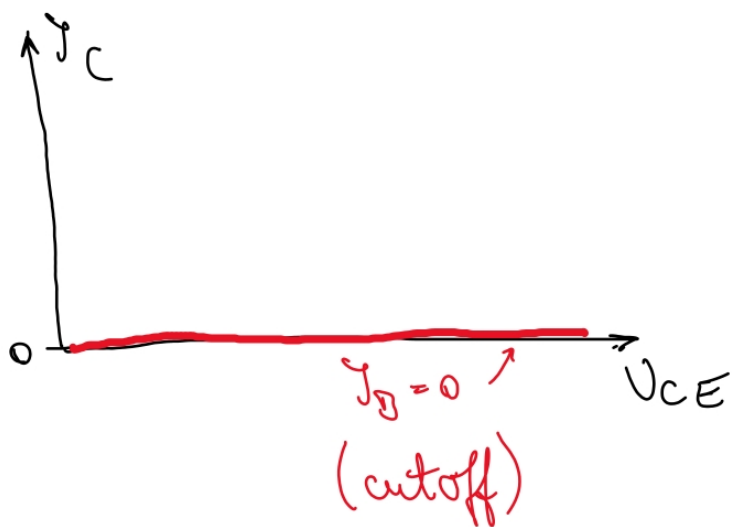
Caracteristicile colectorului: ($I_B = ct.$)




mod blocat:

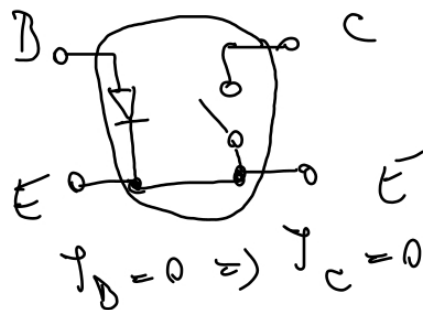



mod activ

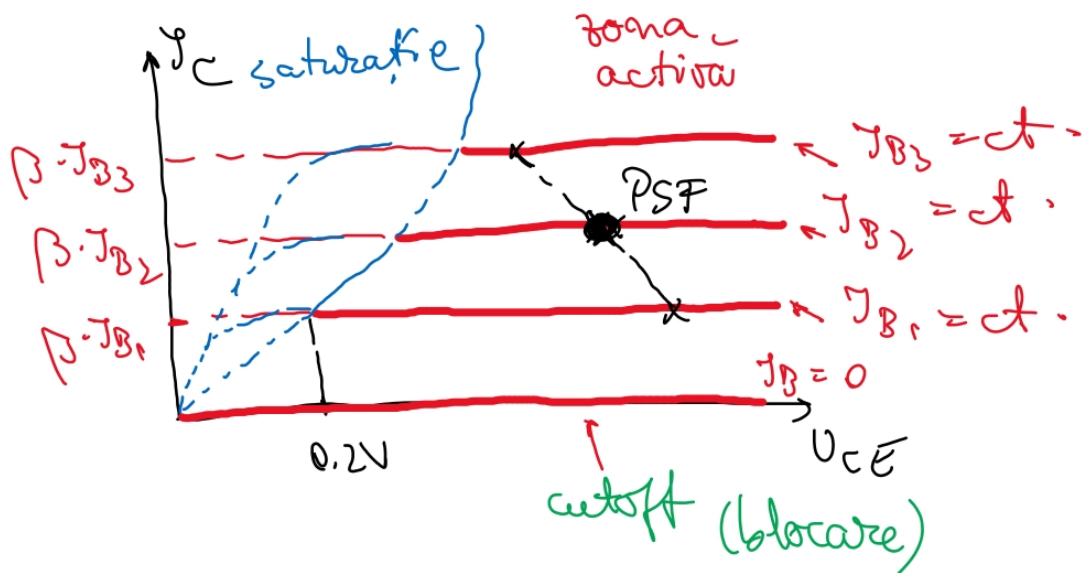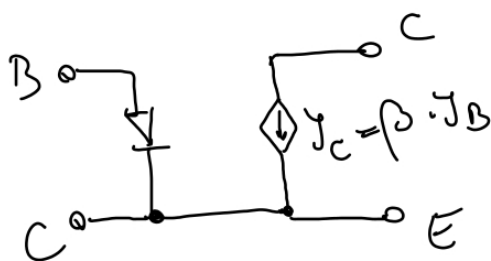

mod saturat

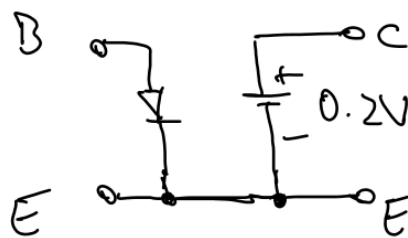

Matricea hibridă:

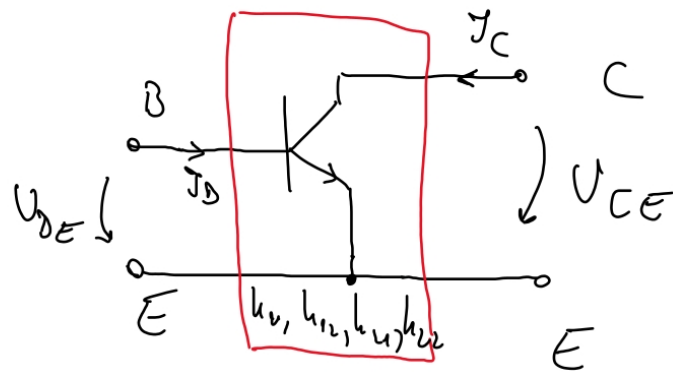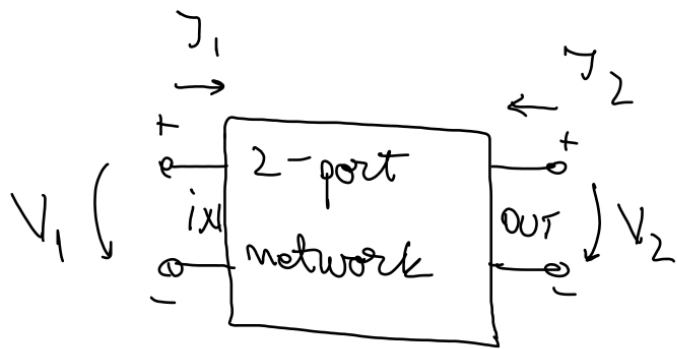

$$\begin{pmatrix} V_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ V_2 \end{pmatrix}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

h_{ij} - det. lin. caract. circuitului

Definiri

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = Z_{in} [\Omega] = h_{ie}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = a_{diam} = h_{re}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \beta = h_{fe} \text{ (adimensional)}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = Y_{out} \text{ } \Omega^{-1} \text{ (S)} = \frac{1}{Z_{out}} = h_{oe}$$

$V_{CE} (V)$	$V_{BE} (V)$	$I_B (\mu A)$	$I_C (mA)$
5	0	0	0
5	0.05V	0	0
...
5.005	0.504	0.06	0.004
5	0.600	1.302	0.2
...
4.998	0.650	8.101	1.432
;	;	;	;

$$I_C = f(I_B) \mid V_{CE} = \text{const.} \Rightarrow h_{ie}(h_{11})$$

$$I_B = f(V_{BE}) \mid V_{CE} = \text{const.} \Rightarrow h_{fe}(h_{21})$$