

Seminar 3:

P2.

diodă reală

PSF  $\rightarrow I_D^{DC} = 2.5 \text{ mA}$   
 $U_D^{DC} = 0.7 \text{ V}$

$U_{pol} \rightarrow DC$

Suprapus peste  $U_{pol}$ :

$u_d(t) = 10 \sin \omega t \text{ mV} = U_D^{AC}$


$i_d(t) = ?$

$u_d(t) = ?$

pt. diode uzuale

putem aproxima

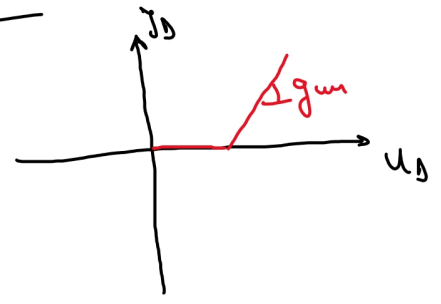
$g_m = 40 \cdot i_d \frac{\text{mA}}{\text{V}}$



$g_m = 40 \times 2.5 \frac{\text{mA}}{\text{V}} = 100 \text{ mA/V} = 0.1 \frac{\text{A}}{\text{V}}$

AC  $\rightarrow$  model practic

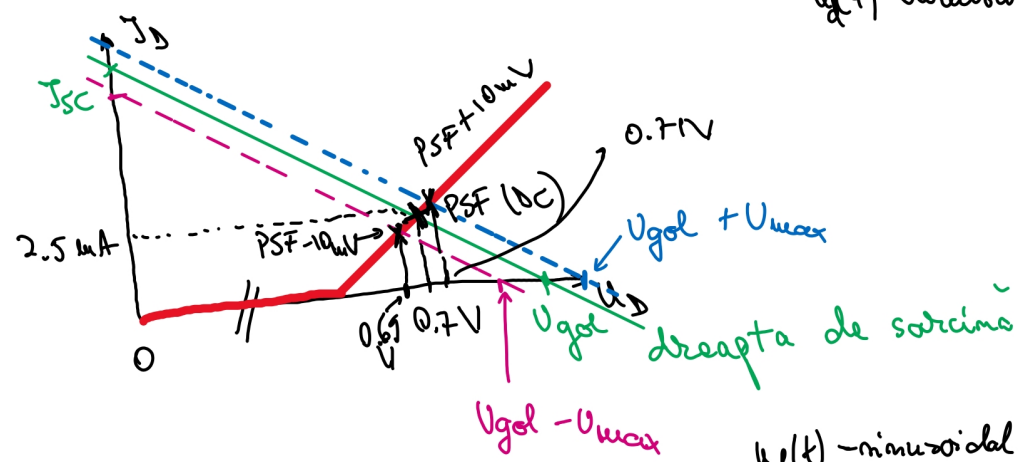$u_d(t)$  variabil  $\rightarrow i_d(t)$  variabil



$u_d(t)$  - sinusoidal (nu avem elemente reactive (C, L))

$i_d = I \cdot \sin \omega t$

$u_d(t) = r_d \cdot i_d(t) \Rightarrow$


$\Rightarrow i_d(t) = \frac{1}{r_d} \cdot u_d(t)$

$i_d(t) = g_m \cdot u_d(t)$

$I \sin \omega t = 0.01 (\sin \omega t) \cdot g_m$

$I = 0.01 \cdot g_m \rightarrow$  amplitudinea lui  $i_d(t)$

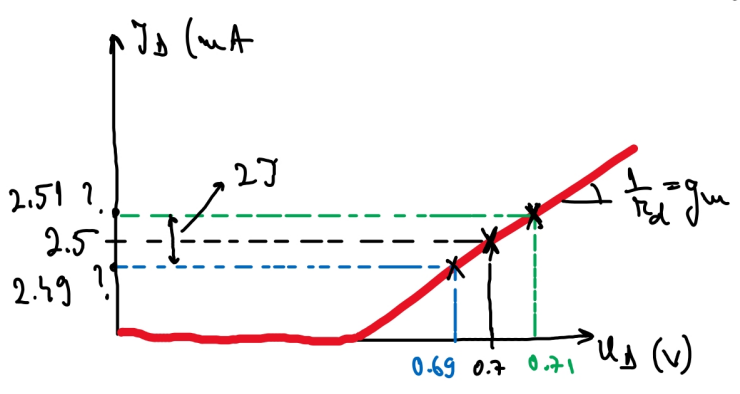$I = 0.01 \times 0.1 = 0.001 \text{ A} = 1 \text{ mA}$



$i_d(t) = \sin \omega t \text{ (mA)}$



P3

$$U_{des} = 0.7V$$

$$g_m = 100 \mu A/V$$

$$I_D = ?$$

$$R = 1k \Omega$$

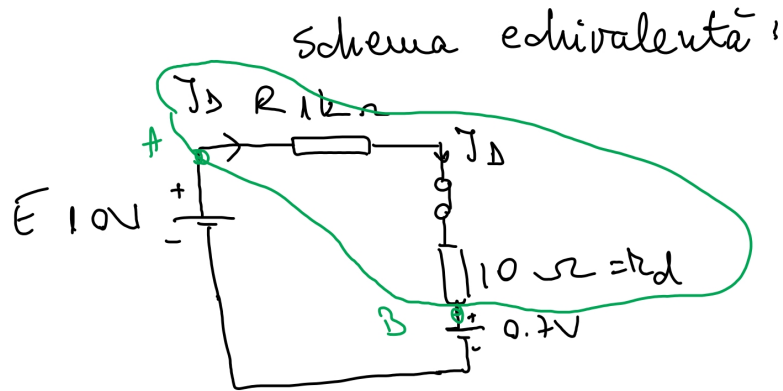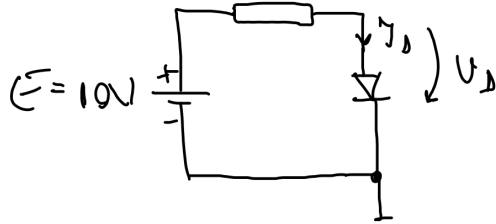

$$V_A = 10V$$


$$V_B = 0.7V$$

$$V_A - V_B = I_D (R + r_d)$$

$$10 - 0.7 = I_D (1000 + 10) =$$

$$\Rightarrow I_D = \frac{9.3V}{1010 \Omega} = 9.2 \mu A$$

folosim modelul practic

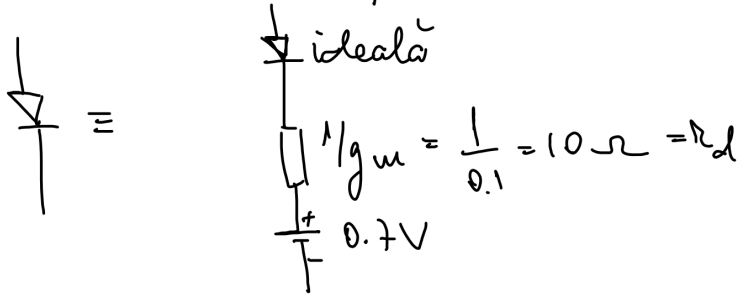



94.

$$V_{out} = f(V_{in})$$

$(V_{in} \in -32 \rightarrow 32 \text{ V})$


Param. diodă:
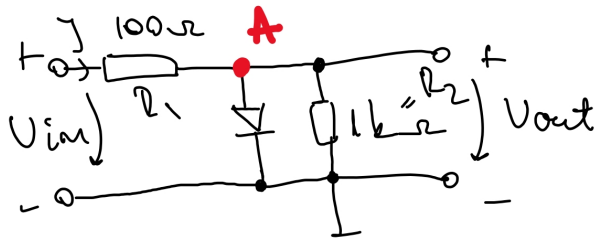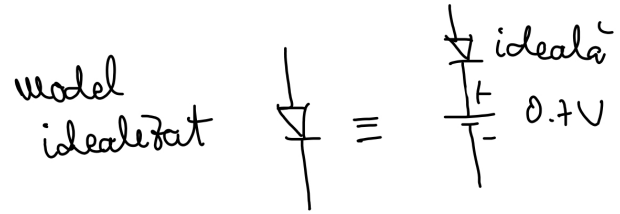
$$\left. \begin{array}{l} U_{des} = 0.7 \text{ V} \\ r_d = 0 \end{array} \right\} \Rightarrow \text{modelul idealizat}$$



$V_{in} = 7$  a.î.  $V_A = 0.7 \text{ V} = V_{out}$

fără diodă →

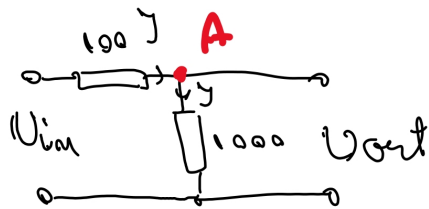

$$\begin{aligned} V_{in} &= 7 \times 1100 \\ V_{out} &= 7 \times 1000 \end{aligned}$$

$$\frac{V_{out}}{V_{in}} = \frac{1000}{1100} \Rightarrow$$

$$\Rightarrow V_{out} = V_{in} \times 0.91$$

Dacă  $V_{out} = 0.7 \text{ V} = V_A$

$$0.7 \text{ V} = V_{in} \times 0.91 \Rightarrow$$

$$\Rightarrow V_{in} = \frac{0.7}{0.91} = 0.77$$

$$-32 \leq V_{in} < 0.77 \text{ V} \Rightarrow V_{out} = V_{in} \times 0.91$$

$V_A \geq 0.7 \text{ V} \rightarrow$  diodă în circuit

