
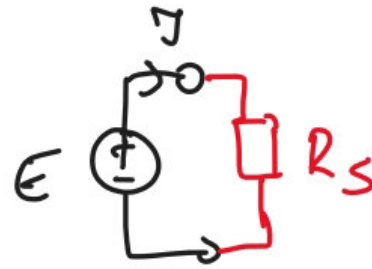


Lab electronica I:

Sursa de tensiune:

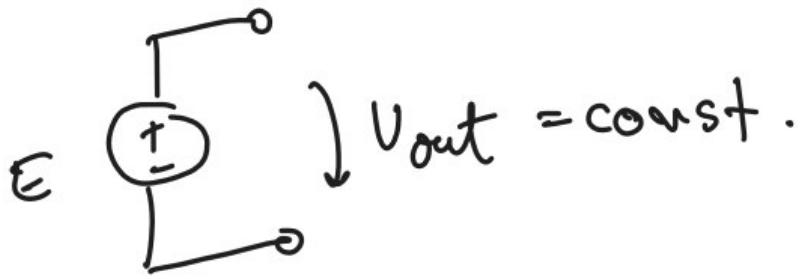

$$E = R_S \cdot J$$

$$E = 10V$$

$$R_S = 1k\Omega$$

$$J = \frac{E}{R_S} = \frac{10V}{1k\Omega}$$

$$= \frac{10V}{1000\Omega} = 0.01A =$$

$$= 10mA$$

$$R_S = 1\Omega \quad J = 10A$$

$$R_S = 0.1\Omega \quad J = 100A$$

$$R_S = 0.01\Omega \quad J = 1000A$$

Sursa de tensiune **REALĂ**

$J \rightarrow J_{max} = \text{finit}$


IDEALĂ

$J_{max} \rightarrow \infty$

$$J_{max} = \underline{\underline{0.1A}}$$

$$E = 10V$$

$$R_S = 1\Omega$$

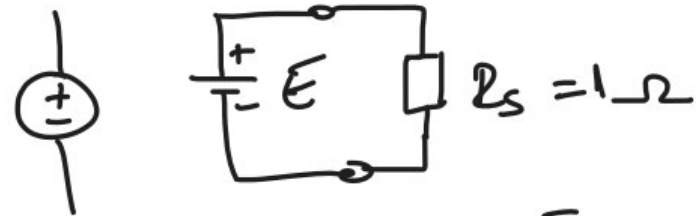


$$\text{ideal } J = \frac{E}{R_S} = \frac{10V}{1\Omega} = 10A \quad !!!$$

$$J_{real}^{max} = 0.1A$$

$$E = R_S \cdot J_{real}^{max} = 1 \cdot 0.1A = 0.1V.$$

Sursa de curent:

IDEALĂ $I_{out} = \text{const.}$

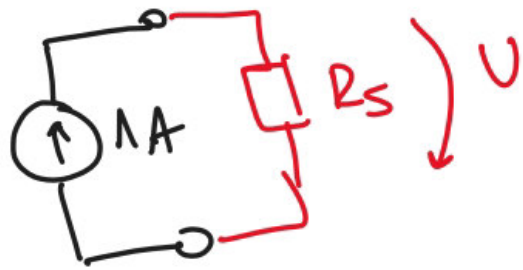

$$U = R_s \cdot I$$

$$R_s = 1 \Omega$$

$$U = 1 \Omega \cdot 1A = 1V$$

$$R_s = 1k\Omega$$

$$U = 1k\Omega \cdot 1A = 1000\Omega \cdot 1A = 1000V$$


Sursa de curent reală:

U_{max}

$$I = 0.1A$$

$$U_{max} = 30V$$

$$R_s = 100 \Omega$$

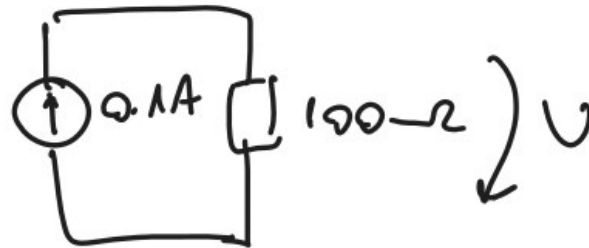

$$U = 0.1A \cdot 100\Omega = 10V$$


$$R_s = 1k\Omega = 1000 \Omega$$

$$U = 0.1A \cdot 1000\Omega = \text{ideal } 100V!$$

$$U_{out} = U_{out}^{max} = 30V$$

$$I = \frac{30V}{1000\Omega} = 0.03A = 30mA$$

Legea lui Ohm

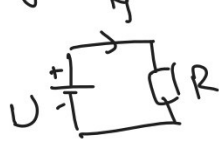


$$U = R \cdot I$$

Kizoltoff:
pt. curenți:

$$\sum I_{in} = \sum I_{out}$$




pt. tensiuni:

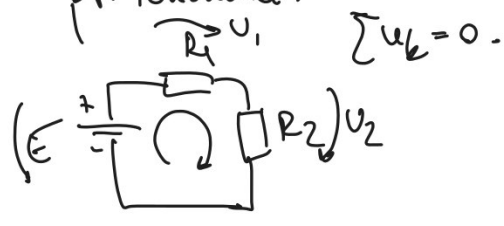

Potential de referință (masă, comun):



$\perp \neq \perp$ EARTH.
(-) ○
○ (+)

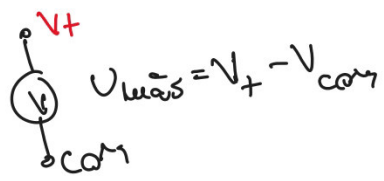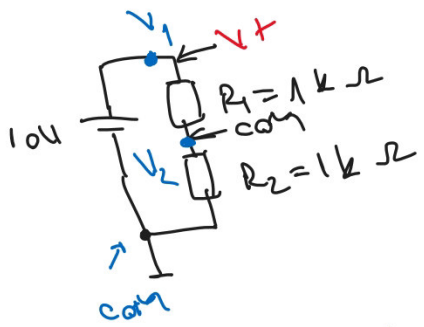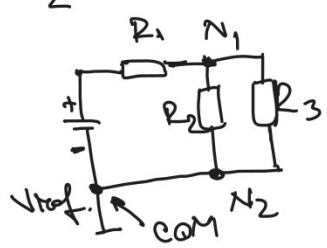

$$U_1 = V_1 - V_{com}$$

$$U_2 = V_2 - V_{com}$$

$$U_R = U_1 - U_2 = V_1 - V_{com} - V_2 + V_{com} = V_1 - V_2$$

