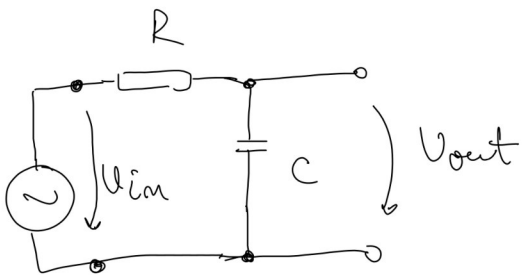


laborator 2 electronica 1:

determinati functia de transfer a filterului de
mai jos.




$$U_{in} = A \sin \omega t$$

$$\frac{U_{out}}{U_{in}} = ? = f(\omega) = \left| \frac{U_{out}}{U_{in}} \right|$$

frecventa, f, ω

Schema echivalenta

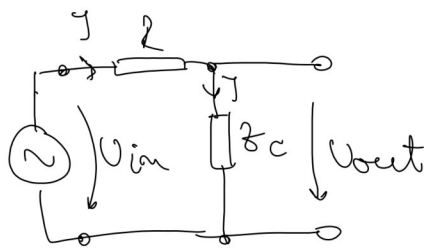

$$U_{in} = I(R + Z_C)$$

$$U_{out} = I \cdot Z_C$$

$$\frac{U_{out}}{U_{in}} = \frac{I Z_C}{I(R + Z_C)} = \frac{Z_C}{R + Z_C} = \frac{Z_C}{Z_C \left(1 + \frac{R}{Z_C}\right)}$$

$$\frac{U_{out}}{U_{in}} = \frac{1}{1 + \frac{R}{Z_C}} = \frac{1}{1 - \frac{R}{j \frac{1}{2\pi f C}}} = \frac{1}{1 - \frac{1}{j} \cdot 2\pi f C R}$$

$$Z_C = -\frac{j}{\omega C} = j \left(-\frac{1}{2\pi f C} \right) \quad \left[\frac{-1}{j} = \frac{1}{j} = j \right]$$

$$\frac{U_{out}}{U_{in}} = \frac{1}{1 + j \cdot 2\pi f R C}$$

$$\left| \frac{U_{out}}{U_{in}} \right|$$

$$\Delta \phi = \phi_{out} - \phi_{in} = 0 -$$

$$\left| \frac{U_{out}}{U_{in}} \right| = \frac{|1|}{|1 + j \cdot 2\pi f RC|} = \frac{1}{\sqrt{1^2 + (2\pi f RC)^2}} = \frac{1}{\sqrt{1 + (f \cdot 2\pi RC)^2}}$$

frecvența de tăiere → atenuare cu 3 dB

$$\left| \frac{U_{out}}{U_{in}} \right| = -3 \text{ dB} = 0.7$$

$$n \text{ [dB]} = 10 \log_{10} \frac{P_{out}}{P_{in}} = 10 \log_{10} \frac{P}{P_{ref}}$$

$$= 10 \log_{10} \frac{\frac{U_{out}^2}{R}}{U_{in}^2 / R} = 10 \log_{10} \left(\frac{U_{out}}{U_{in}} \right)^2 = 20 \log_{10} \frac{U_{out}}{U_{in}}$$

$U_{out} = U_{in} \Rightarrow n = 0 \text{ dB}$ → nici amplificate
nici atenuate

$U_{out} = 2 U_{in} \Rightarrow n = +6.02 \text{ dB}$ amplificate (+dB)

$U_{out} = \frac{1}{2} U_{in} \Rightarrow n = -6.02 \text{ dB}$ atenuare (-dB)

20 log 10

$$\frac{V_{out}}{V_{in}} = -3$$

$$\text{La } f = f_T \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$$


f_T - frequ. de taie
(cutoff frequency)

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (2\pi f_T RC)^2}} = \frac{1}{\sqrt{2}}$$


$$1 + (2\pi f_T RC)^2 = 2$$

$$(2\pi f_T RC)^2 = 1$$

$$f_T = \frac{1}{2\pi RC}$$

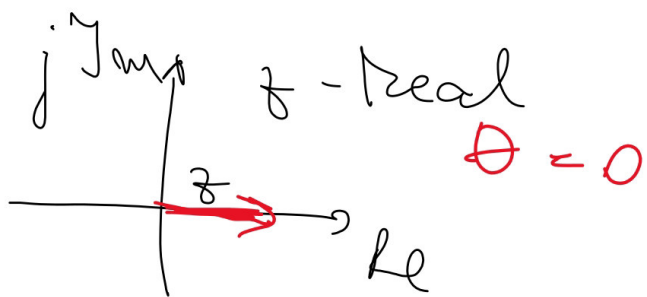

$$\frac{z_1}{z_2} = \frac{|z_1|e^{j\theta_1}}{|z_2|e^{j\theta_2}} = \left| \frac{z_1}{z_2} \right| e^{j(\theta_1 - \theta_2)}$$

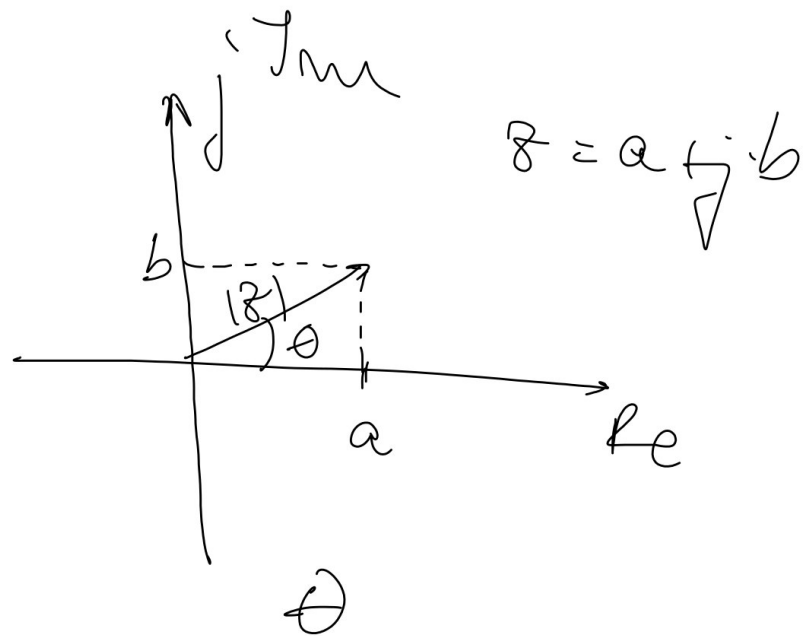

$$\Delta\phi = 0 - \arctan \frac{\text{Re}}{\text{Im}} =$$

$$= 0 - \arctan \frac{1}{2\pi f RC} =$$

$$= -\arctan \frac{1}{2\pi RC f} = -\arctan \frac{f_T}{f} \quad \Delta\phi$$

$$f_T = \frac{1}{2\pi RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_T} \right)^2}}$$