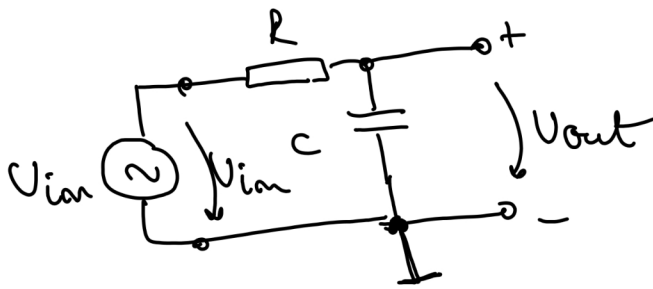


osciloscop nesincronizat
(untriggered)

Trigger



Studiul unui filteru trece-jos (FTJ, LPF) RC;



$\left| \frac{V_{out}}{V_{in}} \right|$ - functia de transfer.

$\left| \frac{A_{out}}{A_{in}} \right|$ - adimensional
- in dB

$\left| \frac{A_{out}}{A_{in}} \right| = f(\text{frec.})$

$n = x \text{ dB}$

$$n [\text{dB}] = 10 \log_{10} \frac{P_{out}}{P_{in}} =$$

$$= 10 \log_{10} \frac{\frac{V_{out}^2}{R}}{\frac{V_{in}^2}{R}} = 10 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)^2 = 20 \log_{10} \frac{V_{out}}{V_{in}}$$


$\Delta \phi = f(\text{frec.})$

$\Delta \phi = \phi_{out} - \phi_{in}$

$V_{out} = V_{in} \Rightarrow n = 20 \log_{10} 1 = 0 \text{ dB}$ (nici atenuare, nici amplificare)

$V_{out} = 2 V_{in} \Rightarrow n = 20 \log_{10} \frac{2 V_{in}}{V_{in}} = 20 \log_{10} 2 = +6.02 \text{ dB}$
(amplificare)

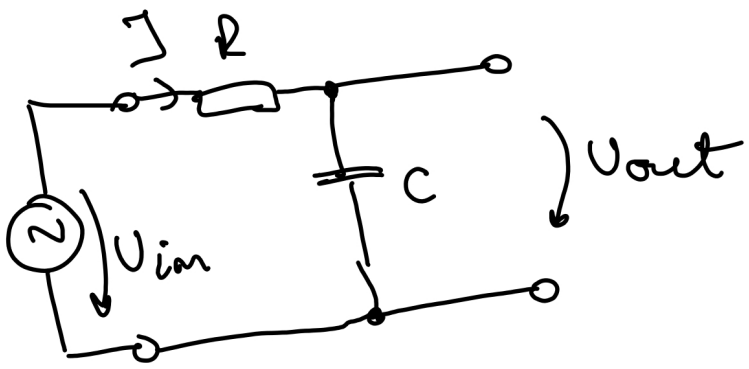$V_{out} = 0.5 V_{in} \Rightarrow n = 20 \log_{10} \frac{0.5 V_{in}}{V_{in}} = -6.02 \text{ dB}$
(atenuare)



$$U_{in} = I(R + Z_C)$$

$$U_{out} = I \cdot Z_C$$

$$\left(\frac{1}{j} = \frac{1}{j} = \frac{j}{j \cdot j} = \frac{j}{-1} = -j \right)$$

$$\Rightarrow \frac{U_{out}}{U_{in}} = \frac{I Z_C}{I(R + Z_C)} =$$

$$= \frac{Z_C}{Z_C \left(1 + \frac{R}{Z_C} \right)} = \frac{1}{1 + \frac{R}{-j \cdot 2\pi f C}} =$$

$$= \frac{1}{1 + j \cdot 2\pi f R C}$$

$$\left| \frac{U_{out}}{U_{in}} \right| = \frac{1}{|1 + j \cdot 2\pi f R C|} = \frac{1}{\sqrt{1 + 4\pi^2 f^2 R^2 C^2}}$$

Frecvența de tăiere:

- frecvența la care $\left| \frac{U_{out}}{U_{in}} \right| = -3 \text{ dB}$

$$20 \log_{10} \left| \frac{U_{out}}{U_{in}} \right| = -3$$

$$\log_{10} \left| \frac{U_{out}}{U_{in}} \right| = -\frac{3}{20}$$

$$\Rightarrow \left| \frac{U_{out}}{U_{in}} \right| = 10^{-\frac{3}{20}} = 0.707 = \frac{1}{\sqrt{2}}$$

$$\text{Dacă } f = f_T \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{1 + 4\bar{u}^2 R^2 C^2 f_T^2}} = \frac{1}{\sqrt{2}} \Rightarrow 1 + 4\bar{u}^2 R^2 C^2 f_T^2 = 2$$

$$4\bar{u}^2 R^2 C^2 f_T^2 = 1$$


$$f_T = \frac{1}{2\bar{u}RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_T}\right)^2}}$$

$$\frac{z_1}{z_2} = \frac{|z_1| e^{j\phi_1}}{|z_2| e^{j\phi_2}} = \left| \frac{z_1}{z_2} \right| e^{j(\phi_1 - \phi_2)}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{1 + j \cdot 2\bar{u}RCf}$$
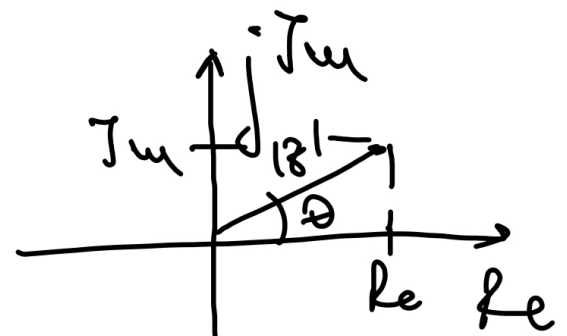
$$\Delta\phi = 0 - \arctg \frac{2\bar{u}RCf}{1} = -\arctg \frac{f}{f_T}$$



$$\text{tg } \theta = \frac{Im}{Re}$$

$$\theta = \arctg \frac{Im}{Re}$$