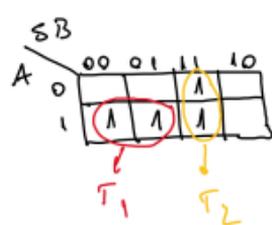


Laborator nr. 5:

$$111 = 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$

MSB LSB MSB LSB


S	B	A	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



S	B	A	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$OUT = T_1 + T_2 = A\bar{S} + SB$$

Schema cu porți: (2x AND, 1x OR, 1x NOT)

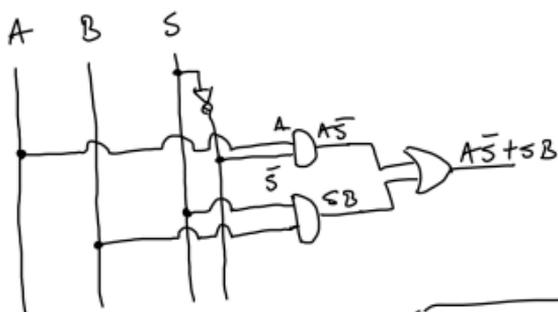



Tabel de adevărit complet pe baza măsurătorilor:

S	B	A	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Multiplexorul funcționează corect.

1c. MUX 4x1:
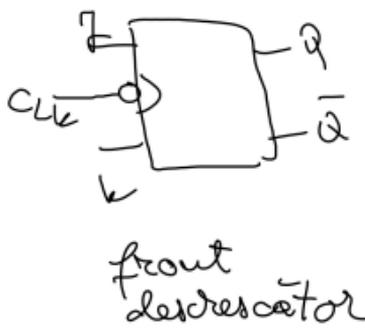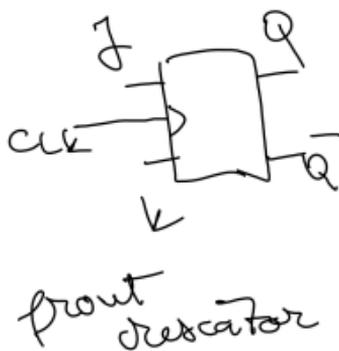
$$OUT = A\bar{S}_2\bar{S}_1 + B\bar{S}_2S_1 + CS_2\bar{S}_1 + DS_2S_1$$



Decoder BCD-decimal pe 2 biți:

Q_1	Q_0	OUT3	OUT2	OUT1	OUT0
0	0	0	0	0	1
1	0	0	0	1	0
2	1	0	1	0	0
3	1	1	0	0	0

$$OUT0 = \bar{Q}_1\bar{Q}_0$$

$$OUT1 = \bar{Q}_1Q_0$$

$$OUT2 = Q_1\bar{Q}_0$$

$$OUT3 = Q_1Q_0$$

$$Q_1 \quad \bar{Q}_1 \quad Q_0 \quad \bar{Q}_0$$

