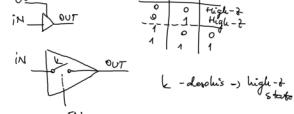


Buffer


in → OUT → OUT = in

Tri-state buffers



3 funcții stocate în ROM


a b c	f_2	f_1	f_0
0 0 0	0	1	(0)
0 0 1	0	1	(1)
0 1 0	1	1	(2)
0 1 1	1	0	(3)
1 0 0	1	0	(4)
1 0 1	0	0	(5)
1 1 0	0	1	(6)
1 1 1	0	0	(7)

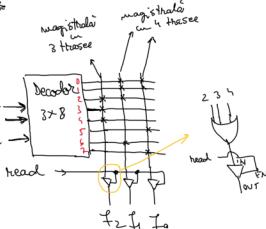


Random access memory (RAM):

- k în adresa
- m output (nr de biti / adresa).
- Dimensiune $2^k \times m$

Schemă bloc

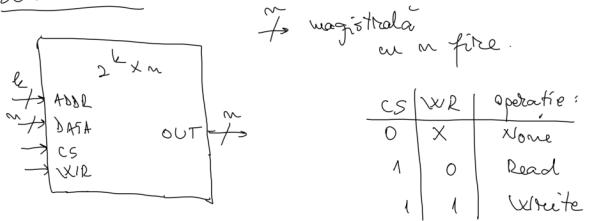


CS	WR	operatie
0	X	None
1	0	Read
1	1	Write

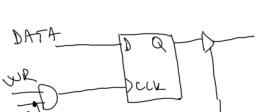

Construcția unei memorii RAM 4×1 (4 biti).

ADDRESS	Data / 1 bit
0	0/1
1	0/1
2	0/1
3	0/1

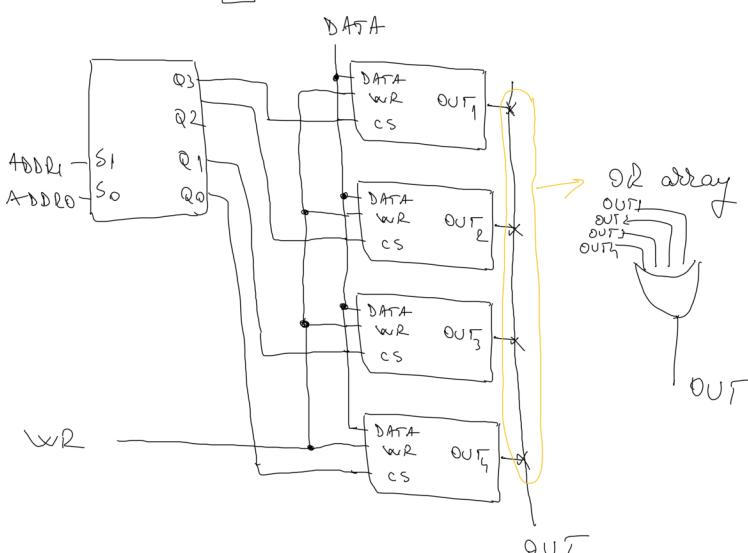→ decodor de adresa + 4 celule RAM de 1 bit.



Tema: Realizati un RAM 4×4 biti folosind un decodator 2×4 și (schemă bloc + implementare în Logisim) celele RAM de 1 bit.