

Diagrama Săuile de admitanță:

Admitanța  $Y_L = \frac{1}{z_L}$  [S, mho]

$$Y_L = G + jS$$

G - conductanța

S - susceptanța


$$\Gamma = \frac{z_L - z_0}{z_L + z_0} = \frac{\frac{z_L}{z_0} - 1}{\frac{z_L}{z_0} + 1} = \frac{z_L - 1}{z_L + 1} \quad \left. \begin{array}{l} \Rightarrow \\ z_L = \frac{1}{y_L} \end{array} \right\} \Gamma = \frac{\frac{1}{y_L} - 1}{\frac{1}{y_L} + 1}$$
$$\Gamma = \frac{1 - y_L}{1 + y_L}$$

$$y_L = \frac{Y_L}{Y_0} = Y_L \cdot z_0 = \frac{z_0}{z_L} = \frac{1}{z_L}$$
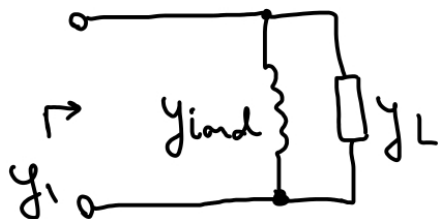
## Efectul unui inductor paralel:

Admitanța inductivă:

$$y_{ind} = \frac{1}{z_{ind}} = \frac{1}{\frac{j \cdot \omega \cdot L}{z_0}} = \frac{-j z_0}{\omega L} = -\frac{j z_0}{2\pi f L}$$




$$y_1 = y_{ind} + y_L = y_L - \frac{j z_0}{\omega L}$$

Efectul  $L$  paralel  $\rightarrow$  deplasare pe cercul de conductanță constantă „counter-clockwise”.

Exemplu de adaptare cu  $L$  paralel:
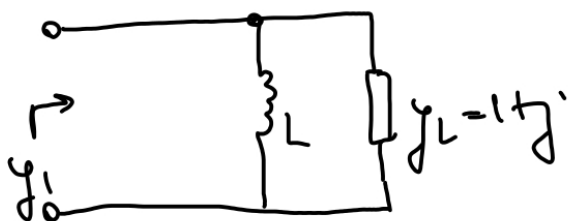
$$y_L = 1 + j \quad ; \quad L = ? \text{ astfel încât } y_1 = 1$$
$$z_0 = 50 \, \Omega \quad ; \quad f = 850 \text{ MHz.}$$



$$y_1 = y_L + y_{ind} = 1$$

$$y_L + y_{ind} = 1$$


$$1 + j - j \frac{z_0}{\omega L} = 1$$

$$-j \frac{z_0}{\omega L} = -j$$

$$z_0 = \omega L \Rightarrow L = \frac{z_0}{\omega} = \frac{50 \, \Omega}{2\pi \times 850 \times 10^6} = 9.36 \text{ nH}$$
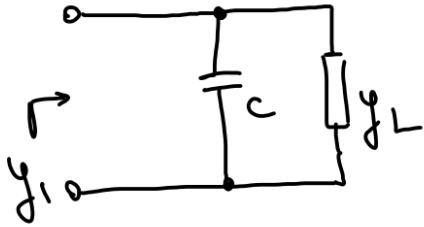
## Efectul capacității paralele:

$$y_c = \frac{1}{z_c} = j \cdot z_0 \cdot \omega C$$



$$y_1 = y_L + y_c$$


$$y_1 = y_L + j z_0 \omega C$$

Efectul C paralel: deplasare pe cercul de conductanță constantă „clockwise”
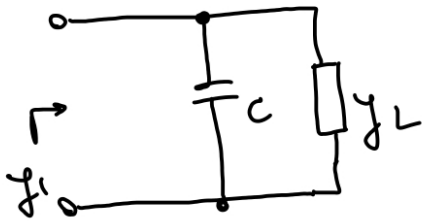
## Exemplu de adaptare cu C paralel:

$$y_L = 0.3 - j0.5 \quad C = ? \text{ astfel încât } y_L = 0.3$$

$$z_0 = 50 \Omega ; f = 2.4 \text{ GHz}.$$



$$y_1 = y_L + y_c = 0.3$$

$$\cancel{0.3} - j \cdot 0.5 + j z_0 \omega C = 0.3$$

$$j z_0 \omega C = j 0.5$$

$$C = \frac{0.5}{z_0 \cdot 2\pi \cdot f} = \frac{0.5}{50 \times 2\pi \times 2.4} \times 10^{-9} =$$

$$= 6.63 \times 10^{-4} \times 10^{-9} = 6.63 \times 10^{-13} \text{ F} =$$


$$= 0.66 \text{ pF}$$

# Adaptarea cu linie de transmisie de scurt :

$$y_L = 0.3 + j \cdot 0.5$$

$$Z_0 = 50 \Omega; f = 750 \text{ MHz}$$

$$y_1 = 1.$$

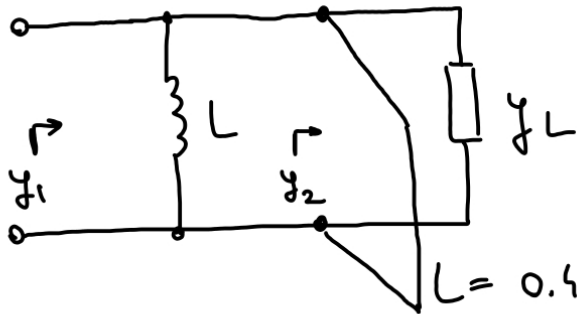

$$L = 0.428\lambda - 0.328\lambda = 0.1\lambda$$

$$y_2 = 1 + 1.6j$$

$$y_1 = y_2 + y_{ind} = 1$$

$$1 + 1.6j - \frac{jZ_0}{\omega L} = 1$$

$$1.6j = j \frac{Z_0}{\omega L} \rightarrow L = \frac{Z_0}{1.6\omega}$$


$$L = \frac{50}{2\pi \times 1.6 \times 750} \times 10^{-6}$$

$$L = 6.63 \text{ nH}$$

# Adaptarea de impedanță față linii de transmisie:

ex:  $z_A = 0.1 - j0.2$  adaptați  $z_A$  față linii de transmisie.

↳ diagrama Smith de impedanță

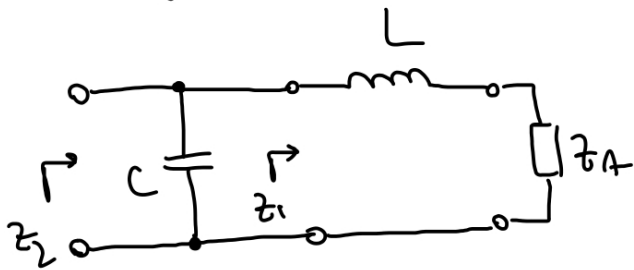

$$f = 16 \text{ Hz}$$
$$z_0 = 50 \Omega$$

$$z_1 = 0.1 + j0.3 = z_A + z_{\text{ind}}$$

$$0.1 + j0.3 = 0.1 - j0.2 + j \frac{\omega L}{z_0}$$

$$j0.3 = j \left( \frac{\omega L}{z_0} - 0.2 \right)$$

$$\frac{\omega L}{z_0} - 0.2 = 0.3$$

$$\frac{\omega L}{z_0} = 0.5$$

$$L = \frac{0.5 \cdot 50 \times 10^{-9}}{2\pi} = 3.98 \text{ nH}$$

$$y_2 = y_1 + y_c = 1$$

$$1 - 3j + y_c = 1$$


$$y_c = 3j$$

$$j z_0 \omega C = 3j \Rightarrow C = \frac{3}{z_0 \cdot \omega} = \frac{3}{2\pi \cdot 50} \times 10^{-9}$$

$$C = 9.55 \text{ pF}$$


# ADMITTANCE SMITH CHART

## Introduction to RF Circuit Design

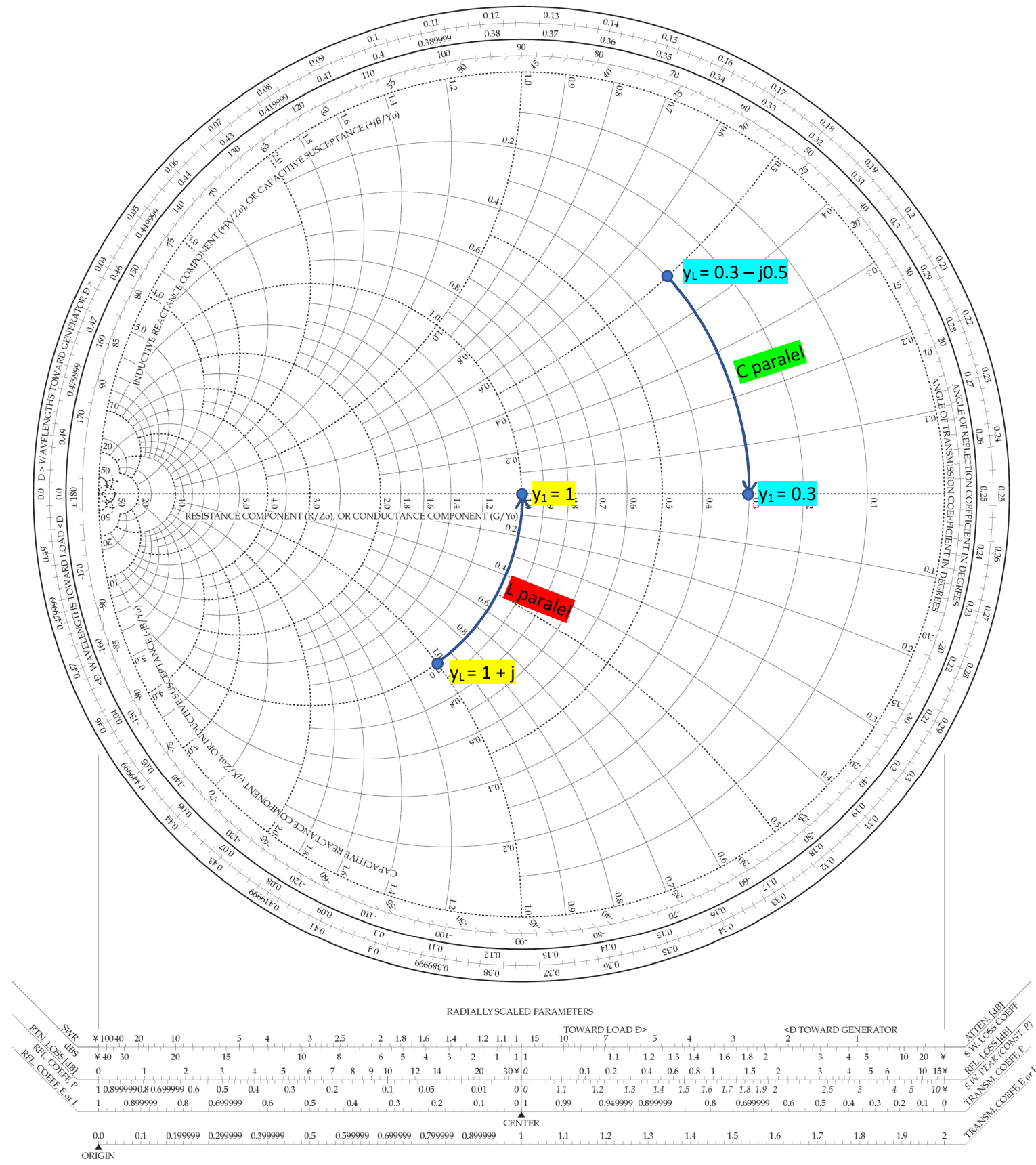

# ADMITTANCE SMITH CHART

## Introduction to RF Circuit Design

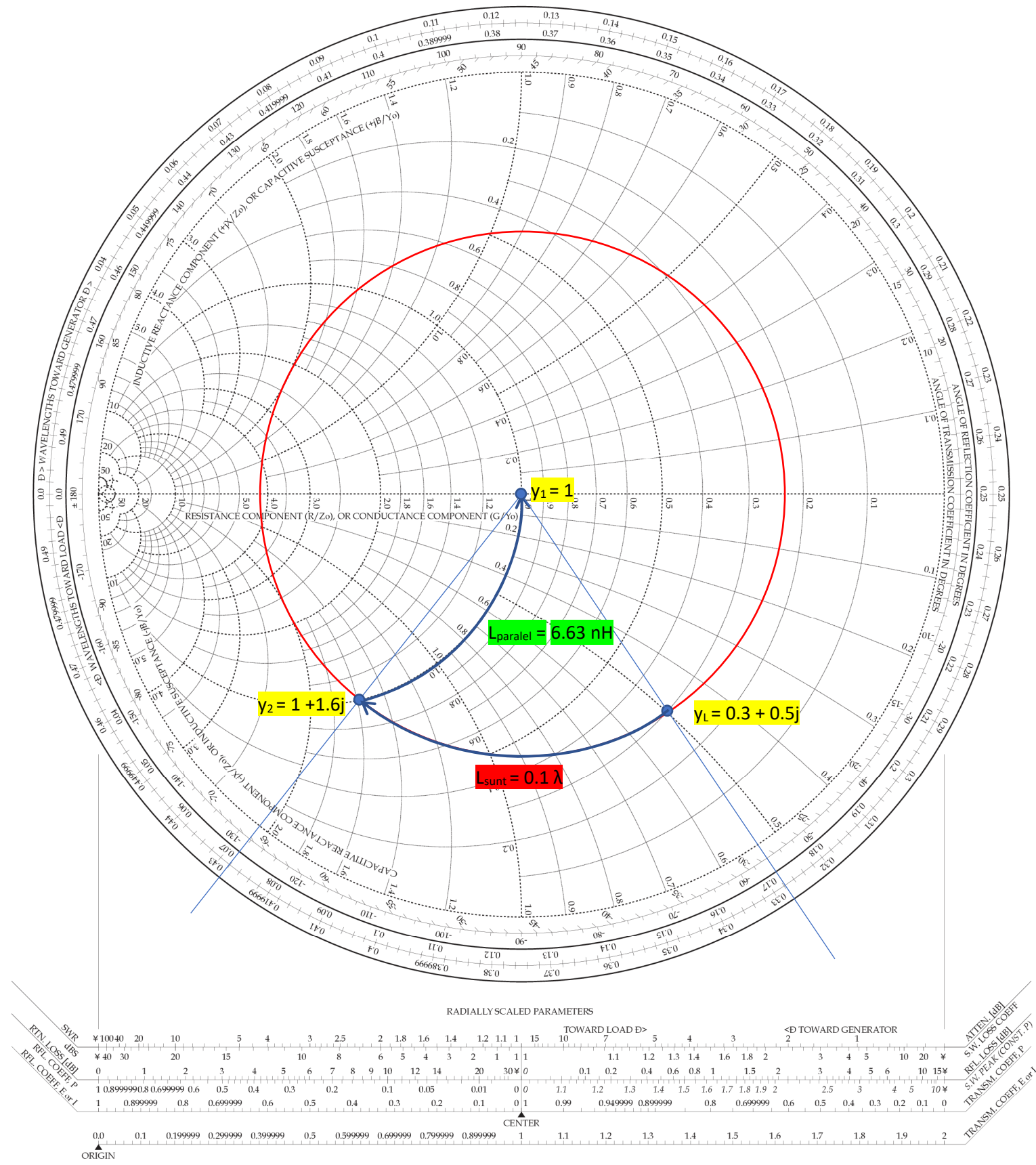

NAME	TITLE	DWG. NO.
SMITH CHART ENGS 120	COLOR BY J. COLVIN, UNIVERSITY OF FLORIDA, 1997	DATE

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

