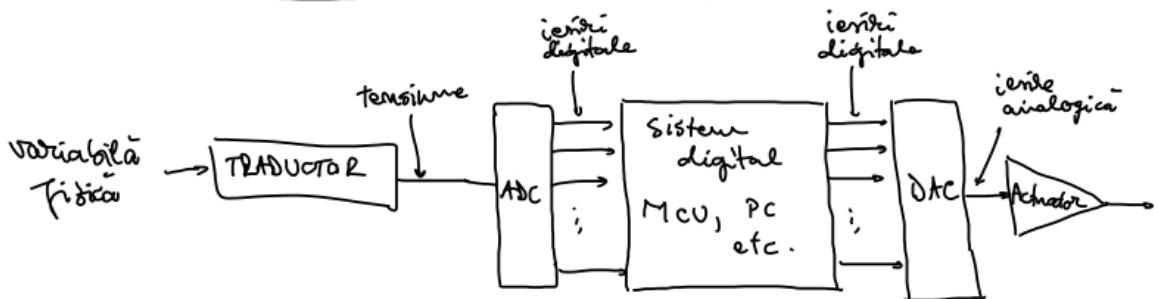


Curs 10 SIS:


## Conversia digital-analogică și analog-digitală;



## Conversia digital-analogică;

DAC = "Digital-to-Analog Converter"

ex: 4 biti.

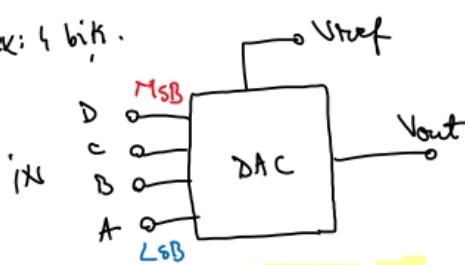

$$V_{out} = k \cdot i_N \text{ digital}$$

$$[k] = V_{ref} / A_{fs}$$

) Full-scale output:  $A_{fs}$

$$\begin{aligned} \text{ex: } V_{ref} &= 15V \Rightarrow \\ &\Rightarrow k = 1V \rightarrow k = f(V_{ref}, I_{ref}) \end{aligned}$$

D	C	B	A	V <sub>out</sub> (V)
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

P1.) DAC pe 5 biti cu output in current

$$I_{out} = 10 \mu A \text{ pt. } i_N = 10100$$

$$I_{out} = ? \text{ dacă } i_N = 11101$$

$$I_{out} = k \cdot i_N$$

$$10 \mu A = k \cdot (1 \cdot 2^4 + 0 \cdot 2^3 + 1 \cdot 2^2 + 0 \cdot 2^1 + 0 \cdot 2^0)$$

$$10 \mu A = k \cdot (2^4 + 2^2) = k \cdot (16 + 4) = k \cdot 20$$

$$k = \frac{10 \mu A}{20} = 0.5 \mu A$$

$$I_{out} = 0.5 \mu A \cdot (2^4 + 2^3 + 2^2 + 2^1) = 0.5 \mu A \cdot (16 + 8 + 4 + 1) =$$

$$\Rightarrow I_{out} = 14.5 \mu A \text{ pt. } i_N = 11101$$

P2.

DAC pe 8 biti ;  $V_{out} = 1V$  pt.  $iN = 00110010$ 

$A_{fs} = ?$

$V_{out} = k \cdot iN$

$1V = k \cdot (2^5 + 2^4 + 2^1) = k(32 + 16 + 2)$

$1V = k \cdot 50$

$k = \frac{1V}{50} = 0.02V = 20mV$

$A_{fs} = V_{out}^{\max} = k \cdot (1111111)$

$A_{fs} = 20mV (2^7 + 2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0) =$

$= 20mV \cdot 255$

$A_{fs} = 5.1V$

### Ponderarea intratilor convertorului digital-analogic

ex.: DAC pe 4 biti cu  $k = 1V$ 

DC BA	$V_{out}$
0001	1V
0010	2V
0100	4V
1000	8V

(P3.)


DAC pe 5 biti ;  $V_{out} = 0.2V$  pt.  $iN = 00001$ 

$A_{fs} = ?$

$A_{fs} = V_{out} \text{ pt. } iN = 11111$

$A_{fs} = 0.2V + 0.4V + 0.8V + 1.6V + 3.2V = 6.2V$


## Rezolutia (step size):

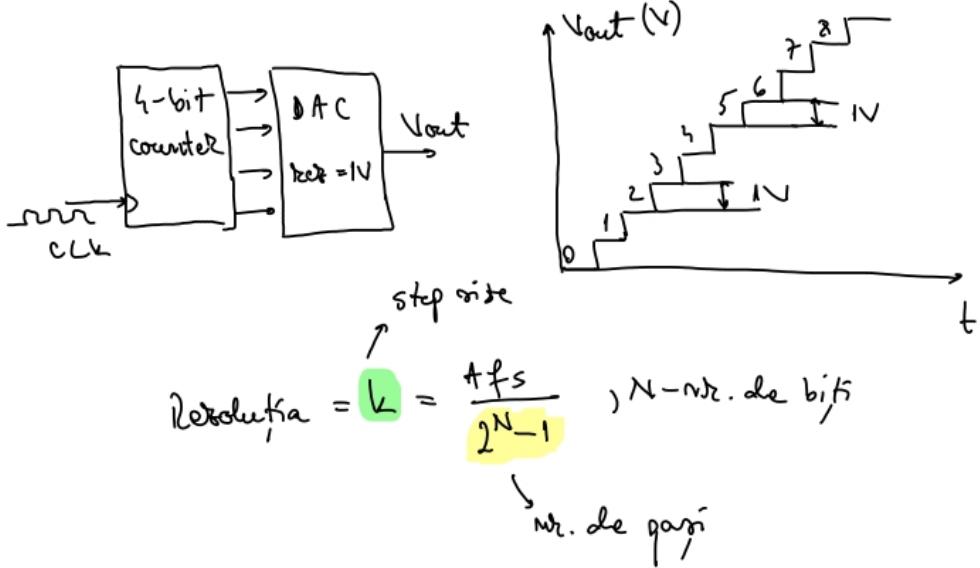

$$\text{Rezolutia (\%)} = \frac{k}{A_{fs}} \cdot 100\% = \frac{1}{2^{N-1}} \cdot 100\%.$$

ex:  $k = 1V$        $\text{Rez. (\%)} = \frac{k}{A_{fs}} \cdot 100\% = \frac{1}{15V} \cdot 100\%$   
 $A_{fs} = 15V$        $= 6.67\%$ .

(24.)

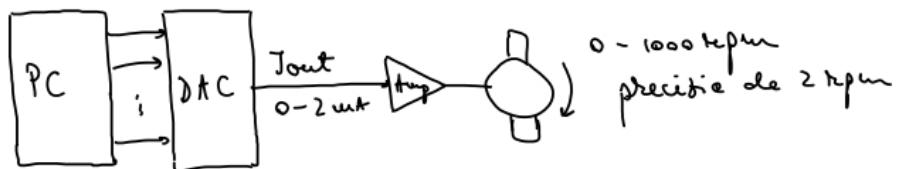

$$\text{Nr. de pasi} = \frac{1000}{2} = 500 \text{ pasi}$$

$$2^{N-1} \geq 500 \rightarrow 9 \text{ biti minimum} \quad \text{--- 512 pasi}$$

$$\text{Nr. de pasi} = 2^9 - 1 = 511 \text{ pasi}$$

$$\text{Precizia} = \frac{1000}{511} = 1.96 \text{ rpm}.$$

DAC cu output negativ

ex: DAC pe 8 biti  $\rightarrow$  MSB = bit de semn

↓  
1 → +  
0 → -

$$11111111 = +V_{ref} \quad 128$$

$$00000000 = 0V \quad 0$$

$$00000000 = -V_{ref} \quad -127$$

Acuratetea  $\rightarrow \gamma_{FS}$

- full-scale error

$$\text{ex: } 0.01\% \text{ FS. } \left. \begin{array}{l} A_{fs} = 9.375V \\ \end{array} \right\} \rightarrow 0.01\% \times 9.375V \Rightarrow \\ \Rightarrow \text{full-scale error} = \pm 0.9375 \mu V$$

- linearity error  $\rightarrow \gamma_{FS}$

$$A_{fs} = 9.375V; \text{ step size } \pm 0.9375 \mu V$$

(P5.) DAC pe 8 biti în curent

$$A_{fs} = 2 \mu A$$

$$\text{full-scale error: } 0.5\% \text{ FS}$$

$$I_{out} = ? \pm ? \quad pt. i_N = 10000000$$

$$k = \frac{A_{fs}}{2^{N-1}} = \frac{2 \mu A}{255} = 7.84 \mu A$$

$$I_{out} = k \cdot 128 \approx 100 \mu A \quad pt. i_N = 10000000$$

$$\text{erroarea} = \pm 0.5\% \times 2 \mu A = \pm 10 \mu A$$

$$I_{out} = 100 \mu A \pm 10 \mu A \quad \begin{matrix} < 99 \mu A \\ > 101 \mu A \end{matrix}$$

Eroarea de offset:

DAC offset error de 2 mV

output ideal 100 mV  $\rightarrow$  real 102 mV

offset error  $\begin{smallmatrix} + \\ - \end{smallmatrix}$


Timp de stabilizare (settling time)

tempul în care  $I_{out}$  se stabilește la  $V_{out}$ ,  $I_{out} \pm \frac{1}{2} k$   
( $\pm 0.5 \text{ LSB}$ )

Monotonicitate:

derivata  $V_{out}, I_{out}$  cu același semn ca și derivata  
maximă de intrare

•) DAC cu 4 biti

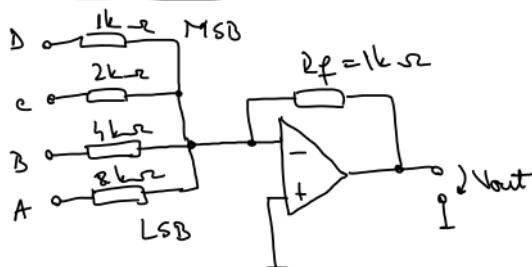

$$V_{out} = - \left( \frac{V_D}{1k\Omega} + \frac{1}{2} \frac{V_C}{2k\Omega} + \frac{1}{4} \frac{V_B}{4k\Omega} + \frac{1}{8} \frac{V_A}{8k\Omega} \right)$$

$$V_{A,B,C,D} = 0; 5V$$

$$A_{f_0} = -5 \left( \frac{\frac{8}{1}}{1} + \frac{\frac{1}{2}}{2} + \frac{\frac{1}{4}}{4} + \frac{\frac{1}{8}}{8} \right) = -\frac{75}{8} = -9.375V$$



$$2k\Omega = \frac{1}{8} \cdot 5V = 0.625V$$

$$k = -0.625V$$


Ponderile intrărilor

D C B A	Vout (V)
0 0 0 1	-0.625
0 0 1 0	-1.25
0 1 0 0	-2.5
1 0 0 0	-5

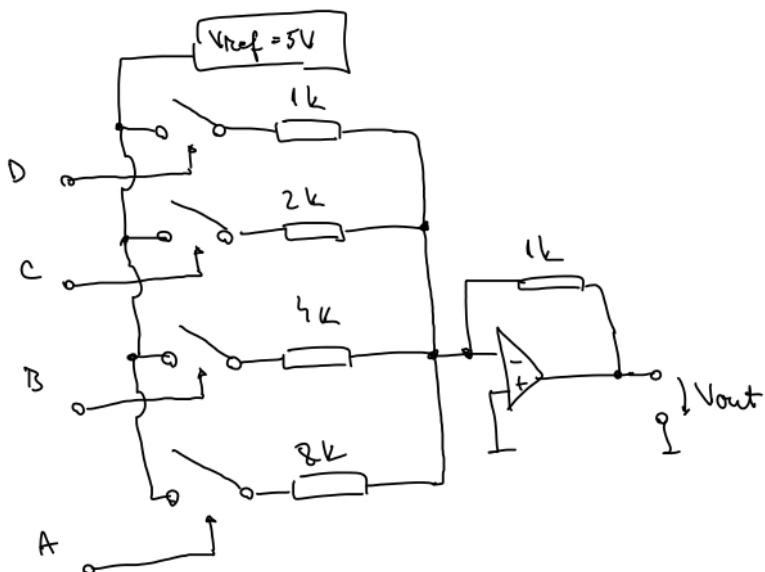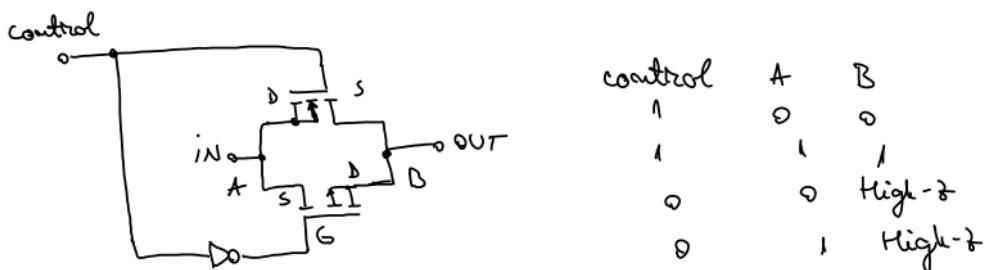switch electronic  $\rightarrow$  poartă de transmisie CMOS




) DAC cu ieșire în curent

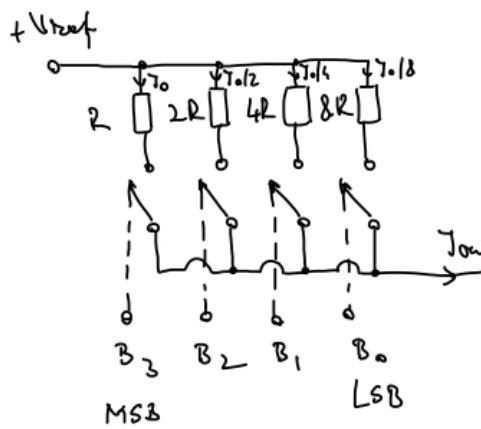

$$J_{out} = B_3 J_0 + B_2 \frac{J_0}{2} + B_1 \cdot \frac{J_0}{4} + B_0 \cdot \frac{J_0}{8}$$

$$J_0 = \frac{V_{ref}}{R}$$

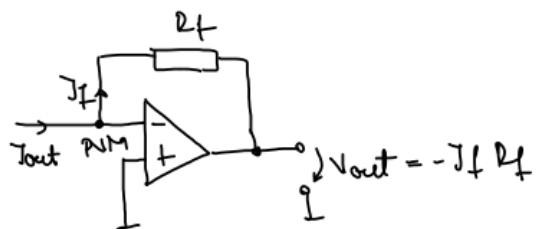

P6.

$$R = 10k\Omega$$

DAC pe 4 biți cu output în curent

$$V_{ref} = 10V$$

$$R_{ef} = ?$$

$$R_L = 0$$

$$A_{fS} = ?$$


$$J_0 = \frac{V_{ref}}{R} = \frac{10V}{10k\Omega} = 1 \mu A$$

$$A_{fS} = J_0 + \frac{J_0}{2} + \frac{J_0}{4} + \frac{J_0}{8} = J_0 \left( 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) =$$

$$= 1.875 \cdot J_0 = 1.875 \mu A$$

$$R_{ef} = \text{ponderare LSB} = \frac{1}{8} \cdot J_0 = \frac{1}{8} \cdot 1 \mu A = 0.125 \mu A$$

) DAC cu scara R-2R

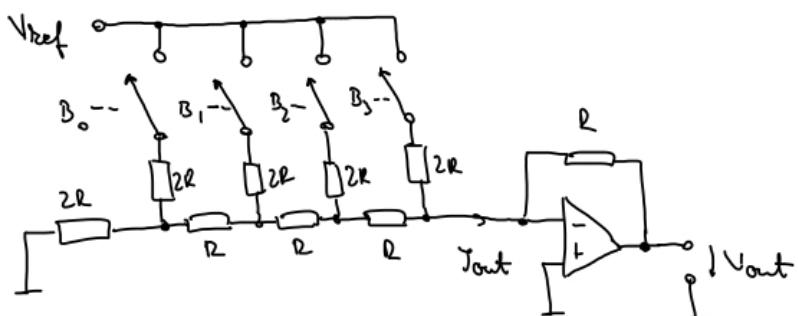

Deducere → la seminat

$$V_{out} = -V_{ref} \left( \frac{B_0}{2^4} + \frac{B_1}{2^3} + \frac{B_2}{2^2} + \frac{B_3}{2^1} \right)$$

LSB

MSB

P7.

DAC R-2R pe 4 biți

$$V_{ref} = 10V$$


$$R_{ref} = ?$$

$$A_{fs} = ?$$

$$R_{ref} = -V_{ref} \cdot \frac{1}{16} = -\frac{10}{16} = -0.625V$$

$$A_{fs} = -V_{ref} \left( \frac{1}{16} + \frac{1}{8} + \frac{1}{4} + \frac{1}{2} \right) =$$



$$= -\frac{15}{16} \cdot 10 = -9.375V$$

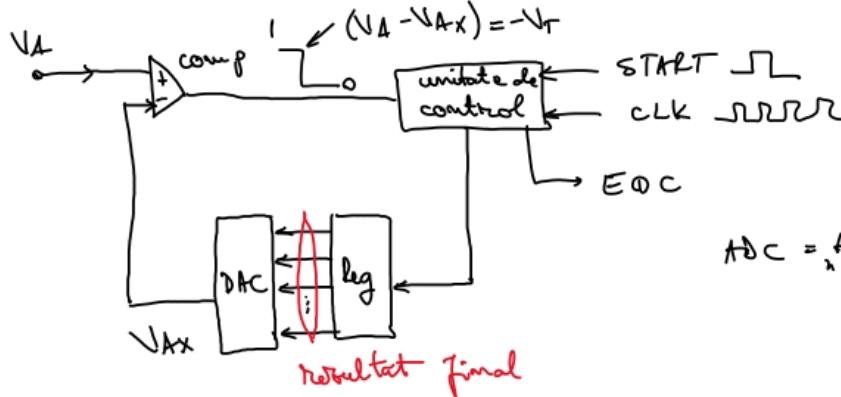Conversie analog-digitală:

ADC = "Analog-to-Digital converter"

.) Convertorul analog-digital cu rampă digitală:

(„digital ramp“ ADC)

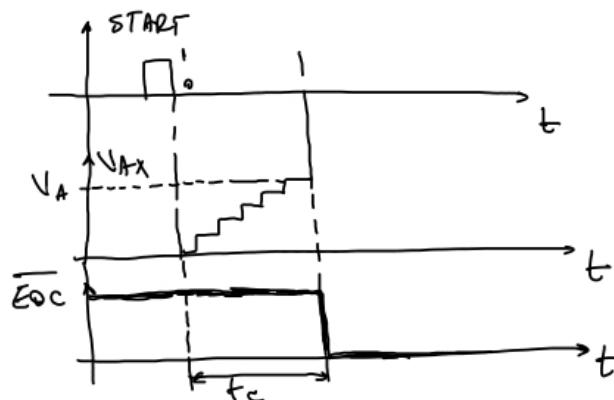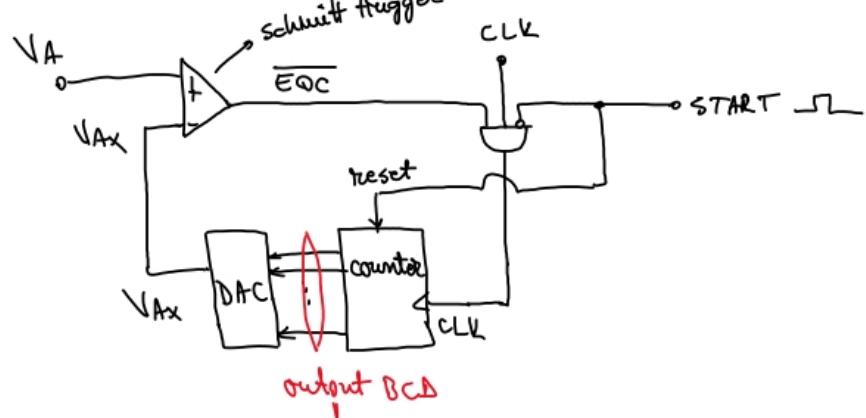

P8.)

$$t_c = ? \quad V_A = 3.728V$$

$$V_{ref} = ? \quad f_{CLK} = 1MHz$$

$$V_T = 0.1mV$$

DAC pe 10 biti  $A_{fs} = 10.23V$

$$\text{nr. de pasi pt. DAC} = 2^{10} - 1 = 1023$$

$$k = \frac{A_{fs}}{2^{10} - 1} = \frac{10.23}{1023} = 10mV$$

||

$$V_{ref} = 10mV$$

$$V_A = 3.728V$$

Basculare Schmitt trigger:

$$V_{th} = V_A + V_T = 3.728V + 0.0001V = 3.7281V$$

$$\text{nr. de pasi} = \frac{3.7281}{10mV} = 372.81 \approx 373 \text{ pasi}$$

$$f = 1MHz \Rightarrow T_{CLK} = 1\mu s \Rightarrow t_c = 373 \times 1\mu s = 373\mu s$$

1) Accurateza ADC im LSB



$$m < 1$$

a) timpul de conversie


$$t_c^{\max} = (2^N - 1) \text{ cicluri CLK}$$

$$t_c^{\text{avg}} = \frac{t_c^{\max}}{2} = 2^{N-1} - 1 \approx 2^{N-1} \text{ cicluri CLK}$$

## ADC cu aproximare succesiune

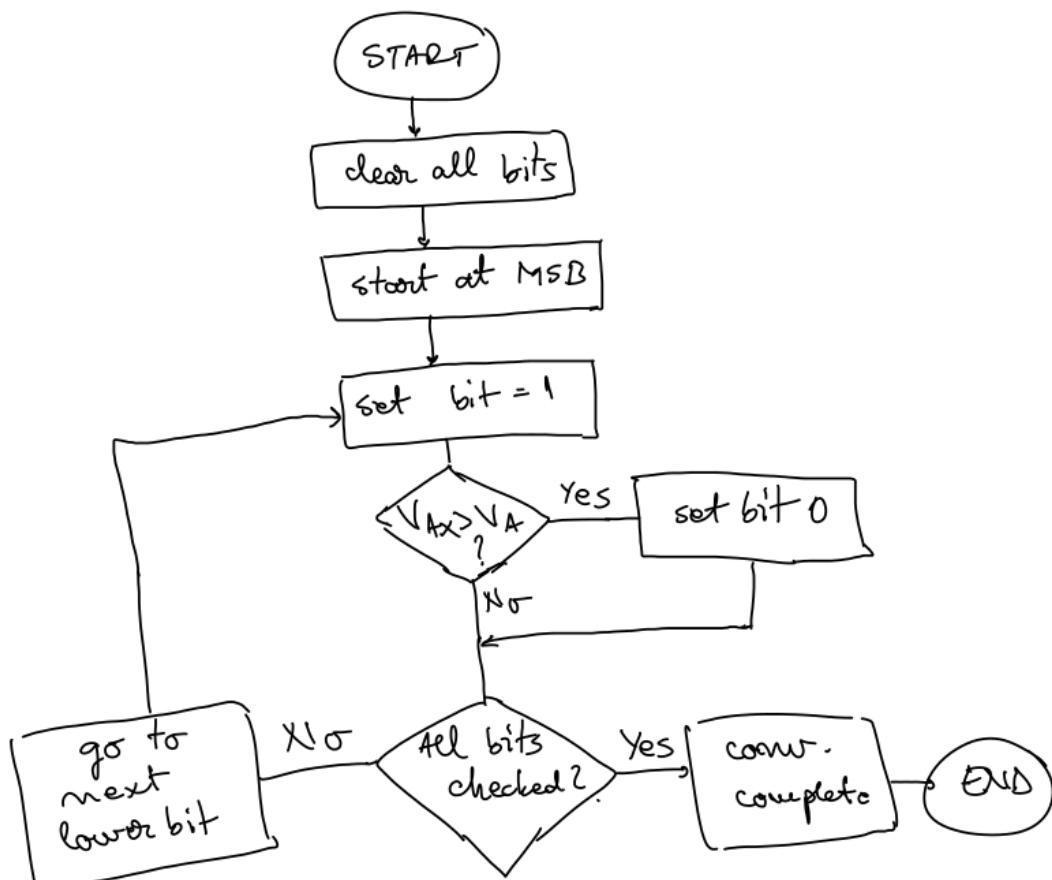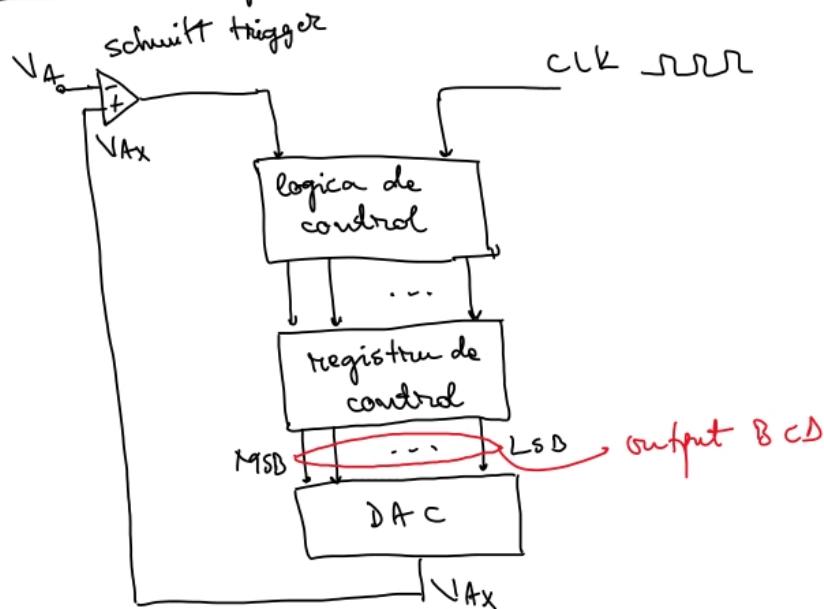

Ex.

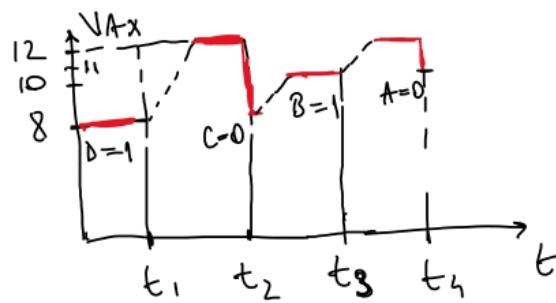

DAC pe 3 biti  
 $k=1V$   
 $V_A = 10.4V$

start  
DC 8 A  
0000  
1000  $t_1$   
1000  $t_2$   
1010  $t_3$   
1010  $t_4$

$$t_c = N \cdot t_{cck}$$

$$t_c = 4 \times t_{cck}$$